

**CDA 4930 002**  
**Digital Circuit Synthesis**  
**Summer 2014**  
**Instructor: Dr. Srinivas Katkoori**  
**Programming Assignment 2 Report**  
**VHDL Behavioral Modeling**

Today's Date:	06/11/14
Your Name:	Mark Little
Your U Number:	84134627
No. of Hours Spent:	20
Exercise Difficulty: (Easy, Average, Hard)	Hard
Any Other Feedback:	

Question 1:

```
-----
-- Company:
-- Engineer:
--
-- Create Date: 18:26:35 06/11/2014
-- Design Name:
-- Module Name: alu - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity alu is
port(ain : in bit;
      bin : in bit;
      cin_add : in bit;
      cin_sub : in bit;
      sel : in bit_vector(1 downto 0);
      cout_add : out bit;
      cout_sub : out bit;
      aout : out bit
    );
end alu;

architecture Behavioral of alu is
```

```

begin

process(sel, ain, bin, cin_add, cin_sub)
begin
    case sel is
    when "00" =>
        aout <= ain xor bin xor cin_add;--adding two integers
        cout_add <= ((bin and cin_add) or (ain and cin_add) or (ain and bin));
    when "01" =>
        aout <= ain xor bin xor cin_sub;--subtracting two integers
        cout_sub <= (((not ain) and bin) or ((not ain) and cin_sub) or (bin and cin_sub));
    when "10" =>
        aout <= ain and bin;--two inputs anded together
    when "11" =>
        aout <= not ain;--inverting input a
    when others =>
        aout <= '0';
    end case;
end process;

end Behavioral;

```

```

-----
-- Company:
-- Engineer:
--
-- Create Date: 18:49:07 06/11/2014
-- Design Name:
-- Module Name: alu8 - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

```

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity alu8 is

port(ain : in bit_vector(7 downto 0);
      bin : in bit_vector (7 downto 0);
      sel : in bit_vector (1 downto 0);
      aout : out bit_vector (7 downto 0)
      );

end alu8;

architecture struct of alu8 is

signal c0 : bit := '0';
signal carout_add, carout_sub, c1, c2, c3, c4, c5, c6, c7, c8, c9,
c10, c11, c12, c13, c14 : bit;

begin

bit0 : entity work.alu(Behavioral)
port map (ain(0), bin(0), c0, c0, sel, carout_add,
carout_sub, aout(0));

bit1 : entity work.alu(Behavioral)
port map (ain(1), bin(1), carout_add,
carout_sub, sel, c1, c2, aout(1));

bit2 : entity work.alu(Behavioral)
port map (ain(2), bin(2), c1, c2, sel, c3, c4, aout(2));

bit3 : entity work.alu(Behavioral)
port map (ain(3), bin(3), c3, c4, sel, c5, c6, aout(3));

bit4 : entity work.alu(Behavioral)
port map (ain(4), bin(4), c5, c6, sel, c7, c8, aout(4));

```

```
bit5 : entity work.alu(Behavioral)
    port map (ain(5), bin(5), c7, c8, sel, c9, c10, aout(5));

bit6 : entity work.alu(Behavioral)
    port map (ain(6), bin(6), c9, c10, sel, c11, c12, aout(6));

bit7 : entity work.alu(Behavioral)
    port map (ain(7), bin(7), c11, c12, sel, c13, c14, aout(7));

end architecture struct;
```

### Question 1: VHDL Testbench

*Where possible test the model exhaustively. If this is not possible, then test with at least 8 different input vectors.*

---

```
-- Company:
-- Engineer:
--
-- Create Date: 19:28:08 06/11/2014
-- Design Name:
-- Module Name: E:/Desktop/School Docs/5/SummerC/CIS 4930-002 Digital Circuit
Synthesis/ass2/redo/alu8_tb.vhd
-- Project Name: redo
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: alu8
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test. Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.
```

---

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;
```

```
ENTITY alu8_tb IS
END alu8_tb;
```

```
ARCHITECTURE behavior OF alu8_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT alu8
```

```

PORT(
    ain : IN  bit_vector(7 downto 0);
    bin : IN  bit_vector(7 downto 0);
    sel : IN  bit_vector(1 downto 0);
    aout : OUT bit_vector(7 downto 0)
);
END COMPONENT;

--Inputs
signal ain : bit_vector(7 downto 0) := (others => '0');
signal bin : bit_vector(7 downto 0) := (others => '0');
signal sel : bit_vector(1 downto 0) := (others => '0');

--Outputs
signal aout : bit_vector(7 downto 0);
-- No clocks detected in port list. Replace <clock> below with
-- appropriate port name

-- constant <clock>_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: alu8 PORT MAP (
        ain => ain,
        bin => bin,
        sel => sel,
        aout => aout
    );

    -- -- Clock process definitions
    -- <clock>_process :process
    -- begin
    --         <clock> <= '0';
    --         wait for <clock>_period/2;
    --         <clock> <= '1';
    --         wait for <clock>_period/2;
    -- end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        --wait for 100 ns;

```

```

--    wait for <clock>_period*10;

-- insert stimulus here
    --test1

    ain <= "00000001";
    bin <= "00000001";

    sel <= "00";

    wait for 60 ns;
    sel <= "01";

    wait for 60 ns;
    sel <= "10";

    wait for 60 ns;
    sel <= "11";

    --test2
    wait for 60 ns;

    ain <= "11111111";
    bin <= "00000000";

    sel <= "00";

    wait for 60 ns;
    sel <= "01";

    wait for 60 ns;
    sel <= "10";

    wait for 60 ns;
    sel <= "11";

    --test3
    wait for 60 ns;

    ain <= "00000001";
    bin <= "11111111";

    sel <= "00";

    wait for 60 ns;
    sel <= "01";

```



```

        wait for 60 ns;
        sel <= "10";

        wait for 60 ns;
        sel <= "11";

--test4
        wait for 60 ns;

        ain <= "00010001";
        bin <= "00010001";

        sel <= "00";

        wait for 60 ns;
        sel <= "01";

        wait for 60 ns;
        sel <= "10";


        wait for 60 ns;
        sel <= "11";

    wait;
end process;

END;

```
 
# Question 1: Simulation Waveforms (add as many pages as you need).



## Question 2:

```
-----
-- Company:
-- Engineer:
--
-- Create Date: 20:04:23 06/11/2014
-- Design Name:
-- Module Name: flipflop - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity flipflop is
port (Clk : in std_logic;
      d : in std_logic;
      d_out : out std_logic
    );
end flipflop;

architecture struct of flipflop is

begin

process(Clk)
begin
```

```

        if(rising_edge (Clk))then
            d_out <= d;
        end if;
    end process;

end struct;

-----
-- Company:
-- Engineer:
--
-- Create Date: 20:10:54 06/11/2014
-- Design Name:
-- Module Name: nbit_reg - Behavioral
-- Project Name:
-- Target Devices:
-- Tool versions:
-- Description:
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-----
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--use IEEE.NUMERIC_STD.ALL;

-- Uncomment the following library declaration if instantiating
-- any Xilinx primitives in this code.
--library UNISIM;
--use UNISIM.VComponents.all;

entity nbit_reg is
    generic (n : integer);
    port (Clk : in std_logic;
          d_out : out std_logic_vector (0 to n-1);
          ind : in std_logic
    );
end nbit_reg;

```

architecture gen of nbit\_reg is

component flipflop

port (Clk : in std\_logic;  
d : in std\_logic;  
d\_out : out std\_logic  
);

end component flipflop;

signal wire1 : std\_logic\_vector(0 to n-1);

begin

flipflop\_a : for i in 0 to n-1 generate  
wire1(i) <= ind;

flipflop\_b : flipflop port map (Clk, wire1(i), d\_out(i));  
end generate;

end gen;

## Question 2: VHDL Testbench

*Where possible test the model exhaustively. If this is not possible, then test with at least 8 different input vectors.*

---

```
-- Company:
-- Engineer:
--
-- Create Date: 20:43:10 06/11/2014
-- Design Name:
-- Module Name: E:/Desktop/School Docs/5/SummerC/CIS 4930-002 Digital Circuit
Synthesis/ass2/redo/nbit_reg_tb.vhd
-- Project Name: redo
-- Target Device:
-- Tool versions:
-- Description:
--
-- VHDL Test Bench Created by ISE for module: nbit_reg
--
-- Dependencies:
--
-- Revision:
-- Revision 0.01 - File Created
-- Additional Comments:
--
-- Notes:
-- This testbench has been automatically generated using types std_logic and
-- std_logic_vector for the ports of the unit under test. Xilinx recommends
-- that these types always be used for the top-level I/O of a design in order
-- to guarantee that the testbench will bind correctly to the post-implementation
-- simulation model.
```

---

```
LIBRARY ieee;
USE ieee.std_logic_1164.ALL;
```

```
-- Uncomment the following library declaration if using
-- arithmetic functions with Signed or Unsigned values
--USE ieee.numeric_std.ALL;
```

```
ENTITY nbit_reg_tb IS
END nbit_reg_tb;
```

```
ARCHITECTURE behavior OF nbit_reg_tb IS
```

```
-- Component Declaration for the Unit Under Test (UUT)
```

```
COMPONENT nbit_reg
```

```

        generic (n : integer := 8);
PORT(
    Clk : IN  std_logic;
    d_out : OUT std_logic_vector(0 to n-1);
    ind : IN  std_logic
);
END COMPONENT;

--Inputs
signal Clk : std_logic := '0';
signal ind : std_logic := '0';

--Outputs
signal d_out : std_logic_vector(0 to 7);

-- Clock period definitions
constant Clk_period : time := 10 ns;

BEGIN

    -- Instantiate the Unit Under Test (UUT)
    uut: nbit_reg PORT MAP (
        Clk => Clk,
        d_out => d_out,
        ind => ind
    );

    -- Clock process definitions
    Clk_process :process
    begin
        Clk <= '0';
        wait for Clk_period/2;
        Clk <= '1';
        wait for Clk_period/2;
    end process;

    -- Stimulus process
    stim_proc: process
    begin
        -- hold reset state for 100 ns.
        wait for 100 ns;

        wait for Clk_period*10;

        -- insert stimulus here

```

```
        ind <= '1';
        wait for 10 ns;
        ind <= '0';
        wait for 10 ns;
        ind <= '1';
        wait for 10 ns;
        ind <= '0';
        wait for 10 ns;
        ind <= '1';
        wait for 10 ns;
        ind <= '0';
        wait for 10 ns;
        ind <= '1';

    wait;
end process;

END;
```



Question 2: Simulation Waveforms (add as many pages as you need).

